

CS 51 Homework 1

Jessie Li

September 21, 2024

Q1

The circuit should output 1 if and only if three of four inputs are 1. Some screenshots of my circuit demonstrating this behavior are shown below:

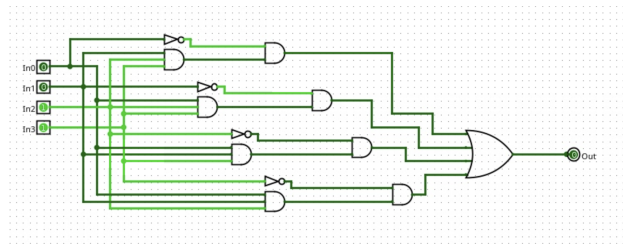


Figure 1: Output should be 0 since only two inputs are 1.

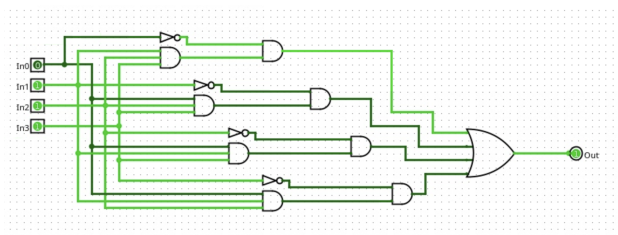


Figure 2: Output is 1 when three of the four inputs are 1.


Testing

To test, I followed [Logisim Test Vectors](#)¹ to create a test vector `test_q1.txt` covering all 16 possible input combinations and verified that the circuit outputs 1 when exactly three inputs are 1, 0 otherwise.

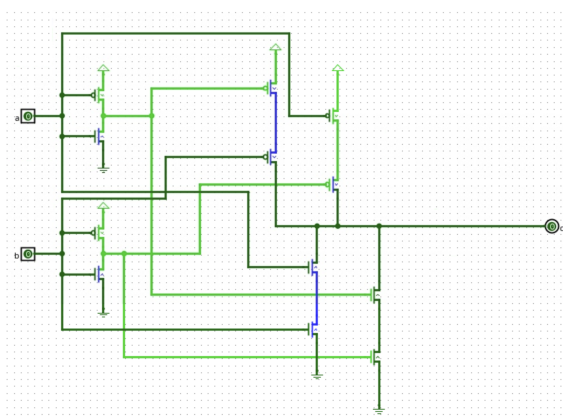
Q2

A


An XOR circuit should output 1 when the two inputs are different (captured by the top half of my circuit) and 0 when they are the same (bottom half of my circuit). My XOR circuit uses 12 transistors in total.




(a) $a = 0, b = 0$ ($c = 0$)

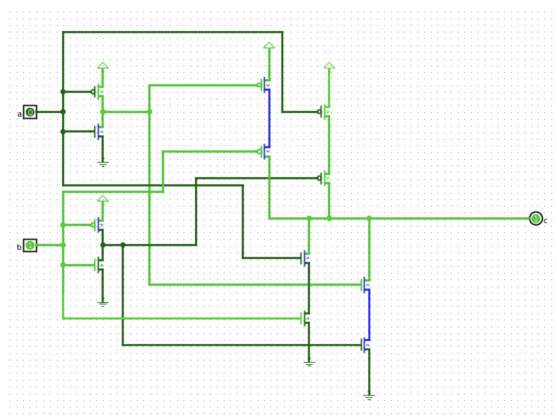

(b) $a = 0, b = 1$ ($c = 1$)

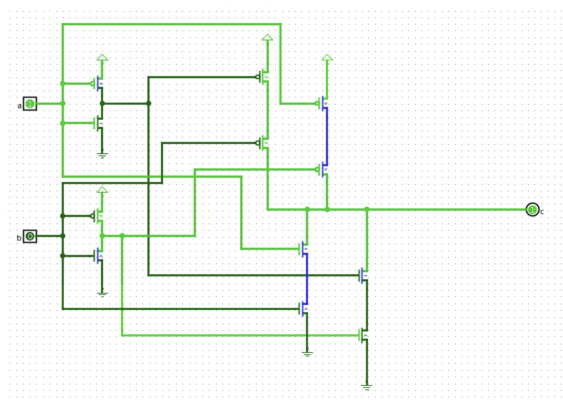

(c) $a = 1, b = 0$ ($c = 1$)

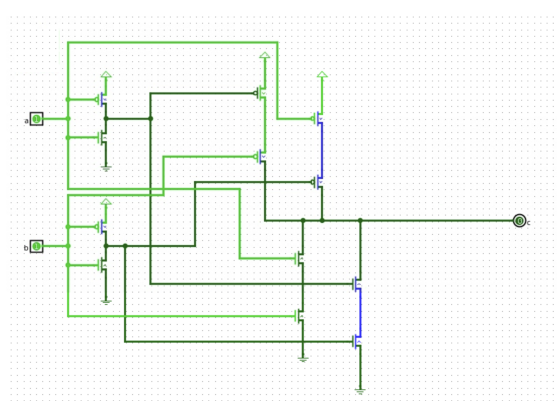

(d) $a = 1, b = 1$ ($c = 0$)

¹www.youtube.com/watch?v=GdDnEPfIXbI

Testing

As in Q1, I loaded a test vector `test_q2.txt` with the four cases shown above to confirm that the output of my XOR circuit was correct for each pair of inputs.

B

In class, we saw that an alternative approach to automated testing was using a counter to iterate through all possible input combinations. For Q2B, I decided to follow [Getting started with Logisim - A Basic Counter](#)² and [Command-line verification](#)³ and hook my XOR subcircuit to a counter to demonstrate its functionality.

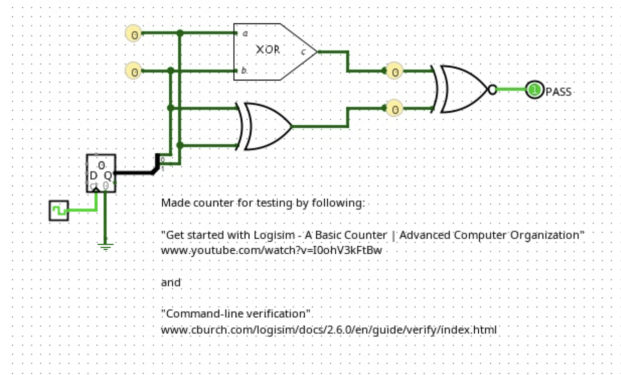


Figure 4: Sample circuit in `main` using my styled XOR circuit.

²www.youtube.com/watch?v=I0ohV3kFtBw

³www.cburch.com/logisim/docs/2.6.0/en/guide/verify/index.html