

CS 51 Homework 3

Jessie Li

October 7, 2024

1.

The design of my 16-byte RAM is based on the 8-nibble RAM in `ram.circ` from the [Fun with Flip Flops](#) lecture. It takes three inputs, `data in` (1 byte wide), `address` (4 bits wide) and a `write` clock (rising-edge triggered), and outputs `data out`.

 


Figure 1: Writing 0xaa to address 0x0.

Testing

I manually verified that my circuit demonstrates the following functionalities:

1. Stores `data in` at the input `address` on the rising edge of the `write` clock.
2. `data out` matches the value stored at `address`.

Here's an example of a sequence I tested:

address	data in	write	data out	description
0x0	0x01	0	0x00	set data in to 0x01 while clock is deasserted
0x0	0x01	1	0x01	write 0x01 to 0x0 on clock rise and show in data out
0x0	0x02	1	0x01	changing data in while clock asserted should not update value at 0x0
0x0	0x02	0	0x01	deassert clock
0x0	0x02	1	0x02	update data at 0x0 on clock rise to 0x02
0x0	0x02	0	0x02	deassert clock
0xf	0x02	0	0x00	change address to 0xf, data out should be 0x00
0xf	0xaa	0	0x00	set data in to 0xaa
0xf	0xaa	1	0xaa	write 0xaa to 0xf
0x0	0xaa	1	0x02	check that 0x02 is still stored at 0x0
0xf	0xaa	1	0xaa	check that 0xaa is still stored at 0xf

2.

For Q2, I created a 16 slot \times 8 bit block of RAM at addresses 0xY0 through 0xYf for a given constant Y. I used a buffer to ensure that **data out** floats if the most significant nibble **MSN** of the address is not equal to Y.

 


Figure 2: RAM chunk for addresses ranging from 0xf0 to 0xff.

Testing

Manual testing confirms the following functionality:

1. **data out** shows the value stored in RAM at the input address when the **MSN** of the address is equal to Y, floating otherwise.
2. **data in** is stored only when the clock rises and the **MSN** = Y.

One sequence I tested with constant Y = 0xf:

MSN	LSN	data in	write	data out	description
0x0	0x0	0x01	0	float	change data in while clock deasserted
0x0	0x0	0x01	1	float	write with MSN \neq Y
0x0	0x1	0x01	1	float	set LSN to 0x1
0xf	0x1	0x01	1	0x00	MSN = Y
0xf	0x1	0x01	1	0x00	set data in to 0x02
0xf	0x1	0x01	0	0x00	deassert clock
0xf	0x1	0x02	1	0x02	write MSN = Y
0xf	0xa	0x02	1	0x00	set LSN = 0xa
0xf	0xa	0xaa	1	0x00	set data in to 0xaa
0xf	0xa	0xaa	0	0x00	deassert clock
0xf	0xa	0xaa	0	0xaa	write 0xaa with MSN = Y
0xe	0xa	0xaa	1	float	set MSN \neq Y
0xf	0xa	0xaa	1	0xaa	check that 0xaa is still stored at 0xfa
0xf	0x1	0xaa	1	0x02	check that 0x02 is still stored at 0xf1

3.

For Q3, I completed the skeletons for `regwriter` and `regreader` to allow:

1. Writing to up to two different registers simultaneously on the rising edge on the clock. **If `reqE` and `reqM` are both asserted and `dstE == dstM`, `valM` is loaded into the register.**
2. Reading two different registers simultaneously, independent of the clock.

Here's a preview of my designs:

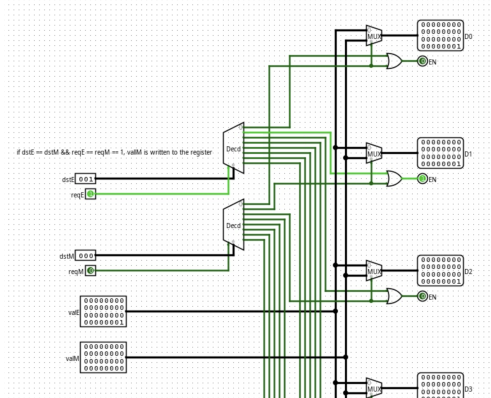


Figure 3: `regwriter`. Decoders determine which register to write to based on `dstE` or `dstM`. `valE` and `valM` are accessible to each output via a MUX, which outputs `valE` if the selection bit (the corresponding output line of M's decoder) is 0, otherwise `valM`. At least one of `reqE` or `reqM` must be asserted for writing to be enabled for a specific register.

 


Figure 4: `regreader`. `srcA` and `srcB` select which registers to read and show the values in `valA` and `valB`.

Testing

To verify correct functionality, these were some of the test cases I covered:

1. **Write to two different registers.** Assert `reqE` and `reqM` with `dstE` \neq `dstM`.
Expect `valE` to be loaded into the register at `dstE` and `valM` to be loaded into the register at `dstM`.
2. **Write to the same register.** Assert `reqE` and `reqM` with `dstE` = `dstM`.
Expect `valM` to be loaded into the register at `dstM` = `dstE`.
3. **Overwrite a previously stored register value.** Pick a register with a previously loaded value for `dstE` and load a new value `valE` into it.
Expect `valE` to replace whatever value was previously stored in the register at `dstE`.
4. **No write to `dstM` when `reqM` is not asserted.** Similarly when `reqE` is not asserted.
Expect the value of the register at `dstM` to stay constant on the rising edge of the clock if `reqM` = 0 and `dstE` \neq `dstM` or `reqE` = 0. However, if `dstE` = `dstM` and `reqE` = 1, expect `valE` to be loaded into the register at `dstE` = `dstM`.
5. **Read from two different registers.** Set `srcA` \neq `srcB`.
Expect `valA` to show the value currently stored in the register at `srcA` and `valB` to show the value currently stored in the register at `srcB`.
6. **Read the same register.** Set `srcA` = `srcB`.
Expect `valA` = `valB` = the value stored in the register at `srcA` = `srcB`.
7. **Clear registers when `clr` is asserted.** Assert `clr` when multiple registers have non-zero values.
Expect all registers to be asynchronously cleared to zero. While `clr` is asserted, registers should be pinned to zero regardless of write attempts.

4.

Q4 asks us to design an ALU for a Y86 processor with 4 operations: `addl` (0x0), `subl` (0x1), `andl` (0x2), and `xorl` (0x3). The ALU takes as input a 4-bit operator `aluOP` and two 32-bit signed two's complement integers `aluA` and `aluB`, and outputs the arithmetic result of `aluB aluOP aluA` in `valE`.

I created two subcircuits to handle addition and subtraction: `addl` and `subl`. Both are responsible for setting the overflow flag `O`.

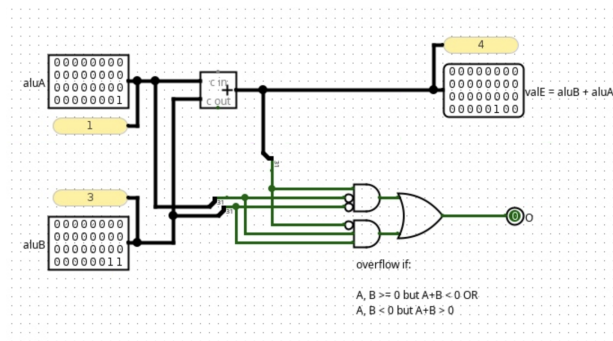


Figure 5: `addl` subcircuit. Overflow `O` is set to 1 if `A` and `B` have the same sign, but the result `valE = A + B` has the opposite. `O` is always zero when `A` and `B` have opposite signs.

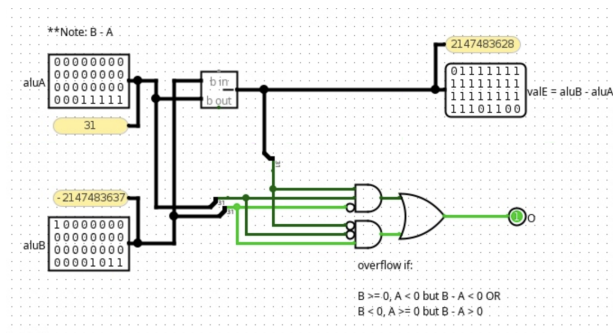


Figure 6: `subl` subcircuit. Note that this circuit computes `B - A`. Overflow `O` is set to 1 if `B < 0` and `A > 0` but `valE = B - A > 0` or if `B > 0` and `A < 0` but `valE < 0`. `O` is always zero when `A` and `B` have the same sign.

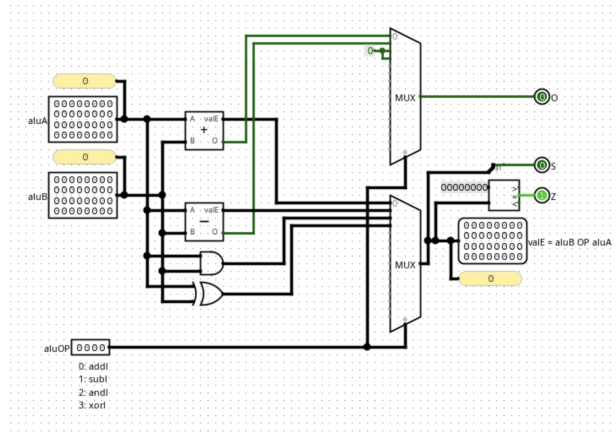


Figure 7: Main circuit with four operations: addition, subtraction, AND, and XOR.

Testing

Some of my test cases are listed on the next page.

aluA	aluB	aluOP	valE	Z	S	O	
0x00000000	0x00000000	0x0 (+)	0x00000000	1	0	0	add
0xffffffff	0x00000001	0x0 (+)	0x00000000	1	0	0	add, zero
0x00000001	0x70000000	0x0 (+)	0x70000001	0	0	0	add two +, no overflow
0xf0000000	0xa0000000	0x0 (+)	0x90000000	0	1	0	add two −, no overflow
0x00000001	0xa0000000	0x0 (+)	0xa0000001	0	1	0	add +/−, no overflow
0x7fffffff	0x00000001	0x0 (+)	0x80000000	0	1	1	add, overflow max
0xffffffff	0x80000000	0x0 (+)	0x7fffffff	0	0	1	add, overflow min
0x00000000	0x00000000	0x1 (−)	0x00000000	1	0	0	sub
0x00000001	0x00000001	0x1 (−)	0x00000000	1	0	0	sub, zero
0x00000001	0x00000002	0x1 (−)	0x00000001	0	0	0	sub two +, no overflow
0xffffffffa	0xffffffffc	0x1 (−)	0x00000002	0	0	0	sub two −, no overflow
0xffffffffe	0x00000001	0x1 (−)	0x00000003	0	0	0	sub B > 0, A < 0, no overflow
0x00000001	0xffffffffe	0x1 (−)	0xffffffffd	0	1	0	sub B < 0, A > 0, no overflow
0x80000001	0x00000001	0x1 (−)	0x80000000	0	1	1	sub, overflow max
0x00000001	0x80000000	0x1 (−)	0x7fffffff	0	0	1	sub, overflow min
0x80808080	0x10101010	0x2 (AND)	0x00000000	1	0	0	and, zero
0x00000001	0x0000000f	0x2 (AND)	0x00000001	0	0	0	and, nonzero
0x80000001	0x8000000f	0x2 (AND)	0x80000001	0	1	0	and, sign
0xffff0000	0xffff0000	0x3 (XOR)	0x00000000	1	0	0	xor, zero
0x00000001	0x00000002	0x3 (XOR)	0x00000003	0	0	0	xor, nonzero
0x40000000	0x80000000	0x3 (XOR)	0xc0000000	0	1	0	xor, sign
0x00000000	0x00000000	0x4 (?)	xxxxxxxx	x	x	x	unknown operator